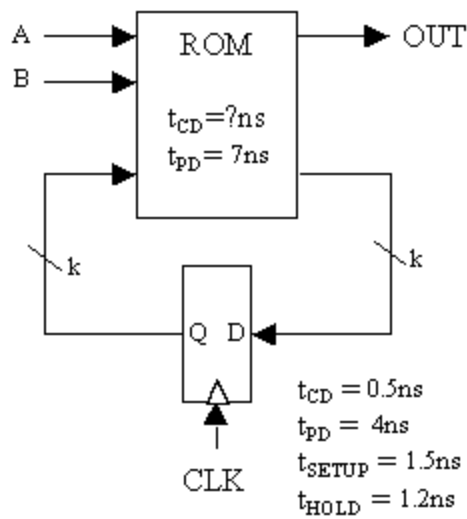


Finite State Machines

When entering numeric values in the answer fields, you can use integers (1000, 0x3E8, 0b1111101000), floating-point numbers (1000.0), scientific notation (1e3), engineering scale factors (1K), or numeric expressions (3*300 + 100).

Problem 1. FSMs


A possible implementation of a finite state machine with two inputs and one output is shown below.



- A. If the register is 5 bits wide (i.e., $k = 5$) what is the appropriate size of the ROM? Give the number of locations and the number of bits in each location.
- Number of locations
- Number of bits in each location
- B. If the register is 5 bits wide what is the maximum number of states in an FSM implemented using this circuit?
- Maximum number of states
- C. What is the smallest possible value for the ROM's contamination delay that still ensures the necessary timing specifications are met?
- smallest possible value for $t_{CD,ROM}$ (in seconds)
- D. Assume that the ROM's $t_{CD} = 3ns$. What is the shortest possible clock period that still ensures that the necessary timing specifications are met?
- smallest clock period (in seconds)

 Problem 2. State Transition Diagram

Shown below is a state transition diagram for an FSM, F, with a single binary input B. The FSM has a single output, a light which is on for the three states marked by a gray dot. The starting state is marked by the heavy circle.



A. Is there a *synchronizing sequence* of inputs which will return this FSM from an unknown state to its starting state?

Synchronizing sequence


- ☐ 00010 is such a sequence
- ☐ 01010 is such a sequence
- ☐ 00000 is such a sequence
- ☐ 11101 is such a sequence
- ☐ No such sequence exists

B. Does this FSM have a pair of equivalent states that may be merged to yield a 3-state FSM?

Equivalent states

- ☐ Yes; the two middle states (upper and lower) are equivalent.
- ☐ Yes; the lower and rightmost states are equivalent.
- ☐ Yes; the leftmost and rightmost states are equivalent.
- ☐ No two states are equivalent; this FSM cannot be reduced.

 C. The following circuit is used to implement the above 4-state FSM:




It is known that the starting state of the 4-state FSM corresponds to 00 on the state variable input, and the **light** output is 1 when the light is to be on. What is the value of the **light** output when all three inputs to the ROM are zero?

Value of **light** output

- ☐ 0 (light off)
- ☐ 1 (light on)
- ☐ Cannot tell from information given

 D. Fill in the unspecified rows of the following truth table so that it implements the state transition diagram. You will need to enter some combination of three zeros or ones in each field. Other characters in the fields (e.g., spaces) will be ignored. Remember the starting state is 00.



S1	S0	B	S1'	S0'	light
0	0	0			
0	0	1			
0	1	0	1	1	1

0 1 1	0 0 1
1 0 0	<input type="text"/>
1 0 1	<input type="text"/>
1 1 0	<input type="text"/>
1 1 1	<input type="text"/>

Problem 3. Design problem: Well-formed parenthesis string checker

In 1936 Alan Turing described the "a-machine", a device that performed computations on a string of symbols according to a simple set of manipulation rules enumerated in the form of a finite-state machine (FSM). The machine consisted of

...an unlimited memory capacity obtained in the form of an infinite tape marked out into squares, on each of which a symbol could be printed. At any moment there is one symbol in the machine; it is called the scanned symbol. The machine can alter the scanned symbol and its behavior is in part determined by that symbol, but the symbols on the tape elsewhere do not affect the behavior of the machine. However, the tape can be moved back and forth through the machine, this being one of the elementary operations of the machine. Any symbol on the tape may therefore eventually have an innings. (Turing, 1948)

We now refer to this device as a Turing Machine (TM) and use it as our definition for what it means to be computable, i.e., we believe (Church's Thesis) that a function is algorithmically computable if and only if it's computable by a TM.

The goal of this lab is write the FSM controller for a TM that checks to see if the string of left and right parentheses it finds on its input tape "balance".

The TM has a doubly-infinite tape with discrete symbol positions (cells) each of which contains one of a finite set of symbols. The control FSM has one input: the symbol found in the current cell. The FSM produces several outputs: the symbol to be written into the current cell and a motion control that determines how the head should move. In our simulation, the tape is displayed horizontally, so the tape can move left, right, or stay where it is.

The operation of the TM is specified by a file containing one or more of the following statements:

```
// comment

C++-style comment: ignore characters starting with the "/" and continuing to the end of the
current line.

/* ... */

C-style comment: ignore characters between "/" and "*". Note that the ignored characters may
include newlines; this type of comment can be used to comment-out multiple lines of your file.

symbols symbol...
```

Declare one or more tape symbols. The symbol "-" (dash) is predefined and is used to indicate that a tape cell is blank. You have to declare symbols you use in an action statement (see below). A symbol can be any sequence of non-whitespace characters not including "/", "\", or the quote character. If you want to declare a symbol containing whitespace, "/" or quote, you must enclose the symbol in quotes. You can have more than one `symbols` statement in your file.

states *state...*

Declare one or more states. There are two predefined states: `"*halt*"` and `"*error*"`. The TM simulation will stop if either of these states is reached. The `"*error*"` state is useful for indicating that the TM has halted due to an unexpected condition. You can have more than one **states** statement in your file. The first state specified by the first **states** statement is the starting state for the TM.

action *state symbol newstate writesymbol motion*

Specify the action performed by the TM when the current state is *state* and the current symbol is *symbol*. First the TM will write *writesymbol* into the current cell of the tape. Then the tape is moved left if `"l"` is specified for the *motion*, right if `"r"` is specified and remain where it is if `"-"` is specified. Finally the current state of the control FSM is changed to *newstate* and the TM searches for the next applicable action. If *newstate* is `"*halt*"` or `"*error*"`, the TM simulation stops. If there is no action specified for the current state and current symbol, the TM enters the `"*error*"` state. Note that you have to declare any symbols or states you use in an **action** statement -- this requirement is helpful in catching typos.

tape *name symbol...*

Specifies the initial configuration of a TM tape, each tape has a name. The various names are displayed as a set of radio buttons at the bottom of the TM animation -- you can select which tape is loaded at reset by clicking on one of the buttons. You can specify which cell of the tape is to be current cell after reset by enclosing the appropriate symbol in square brackets. For example, an initial tape configuration called `"test"` consisting of three non-blank cells with the head positioned over the middle cell is specified by

```
tape test 1 [2] 3
```

If no initial head position is specified, the head is positioned over the leftmost symbol on the tape.

result *name symbol...*

Specifies the expected head position and contents of the tape after the TM has finished processing the initial tape configuration called *name*. This statement is used by the checkoff system to verify that your TM has correctly processed each of the test tapes. Whenever the TM enters the `"*halt*"` state, the final tape configuration is checked against the appropriate result statement if one has been specified and any discrepancies will be reported in the status display at the bottom of the TMSim window.

result1 *name symbol*

Like **result** except that only the current symbol is checked against the specified value.

Here's an example file that defines a control FSM with three states (`s1`, `s2` and `s3`) and two possible tape symbols: `"1"` and `"-"` (recall that the `"-"` symbol is predefined). There is a single tape configuration defined called `"test"` which consists of a blank tape. The final tape configuration is expected to be a tape containing six consecutive `"1"` symbols with the head positioned over the second `"1"`. Note that there is an action declared for each possible combination of the three states and two tape symbols.

```
// 3-state busy beaver Turing Machine example
```


```
// See how many 1's we can write on a blank tape using
// only a three-state Turing Machine
```

```
states s1 s2 s3 // list of state names, first is starting state
symbols 1      // list of symbols (- is blank cell)
```

```
tape test -      // initial tape contents, blank in this case
result test 1 [1] 1 1 1 1 // expected result
```

```
// specify transistions: action state symbol state' write move
//   state = the current state of the FSM
//   symbol = the symbol read from the current cell
//   state' = state on the next cycle
//   write = symbol to be written into the current cell
//   move = tape movement ("l"=left, "r"=right, "-"=stay put)
action s1 - s2      1 r
action s1 1 s3      1 l
action s2 - s1      1 l
action s2 1 s2      1 r
action s3 - s2      1 l
action s3 1 *halt* 1 r
```

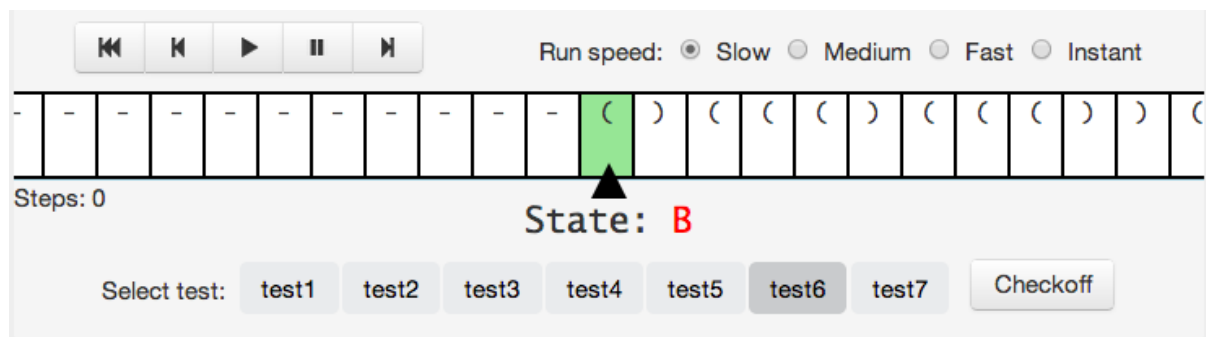You'll find an instance of TMSim, our TM simulator, at the bottom of this webpage. Here's what the TM simulator looks like:



The TM display consists of the following parts:

Simulator control: The five buttons are, respectively:

- reset TM and tape to initial state;
- step back to previous state and tape configuration
- run the simulation for multiple steps
- halt a running simulation
- run the simulation for a single step

The speed of the running machine is determined by the radio buttons on the right.

State display: shows the current tape contents, head position and current state of the controlling FSM. The number of simulation steps is displayed on the left, just below the tape. The next action to be performed, as determined by the current state and tape symbol, is highlighted in your design file.

Test selection: radio button to select which test tape to use. A **Checkoff** will also be displayed. Clicking on **Checkoff** will run all the test tapes and, if they all pass, you'll be able to submit your design file online.

Well-formed parenthesis string checker

Your task is to write the control FSM for a TM that determines if the parenthesis string on its input tape is balanced. The initial position of the head will be at the leftmost non-blank symbol on the tape, i.e., at the left end of the parenthesis string. Your TM should halt with a current symbol of "1" if the parens balance, or a current symbol of "0" if the parens don't balance. The head should be positioned over the "0" or "1" on the tape. Note that there are no constraints on what the rest of the tape contains.

NOTE: TMs that simply use some fixed number of states to count the number of unmatched open parentheses would not be able handle an arbitrary-length inputs and so do not qualify as acceptable solutions. The staff will check this constraint during the check-off meeting.

Use the TMSim simulator below to enter your design in the "Paren Checker" tab. The initial contents of the tab are a sequence of test tapes which must be processed successfully by your TM. To run the tests, click "TMSim Assemble" and then "Checkoff". If all the tests pass, then clicking

Check & Save will give you credit for completing this problem. Please see the note on scoring at the end of this problem.

To enable the online system to check this answer, first run the design tests provided by the tool.
Open TMSim in a new window

Note that you're welcome to add your own test tapes while debugging your implementation, but you'll need to comment them out before running the checkoff tests (otherwise the checksum mechanism will get confused).


Scoring: The number of points you'll receive at the Check-off meeting is determined by the number of states in your TM definition:

- 4 points: 2 states
- 3 points: 3 states
- 2 points: 4 states
- 1 point: 5 or more states

"Counting" solutions do not receive any credit.

 Problem 4. Design problem: Sequential Logic

Your task is to design a sequential logic circuit that implements the FSM shown in the state transition diagram below:



The sequential circuit has three inputs:

- **CLK**. One rising clock edge the FSM should advance to the next state which is determined from current state, the RESET input and the IN input.
- **IN**. A simple binary input that determined which, along with the current state, selects which transition is chosen from the state transition diagram.
- **RESET**. When 1 at the rising edge of CLK, the FSM should transition to the SA state regardless of the current state and value of IN.

In the test, the values of IN and RESET are provided 10ns before the rising edge of CLK, which should provide sufficient time for them to be processed by logic or a ROM and influence the value for the next state.


The values of the two outputs, U and V, are determined by the current state and are as shown in the state transition diagram.

The details of the implementation are up to you. Of course, you'll need some number D registers to hold the current state. The next-state and output logic could be logic gates (see L06 slides 23 and 24) or our "standard" ROM plus register setup (see L06 slide 11).

The steps you'll need to follow to complete the design are outlined on slides 8 and 9 of L06. See the diagram on slide 11 of L06 for one way to handle setting an initial state during reset.


The Memory component can be used to build a read-only memory (ROM). You can insert a memory component into your schematic by clicking on the "MEM" icon in the schematic tab and dragging it onto the schematic. Double-click the memory component to change its properties. Please see the documentation for the Memory component at the end of the Standard Cell Library datasheet.

 To build a ROM, set the memory component to have a single port with the desired number of address inputs and data outputs. Connect its CLK and WE inputs to 0'1, which will disable the ability to write into the memory, making it read-only. And connect its OE input to 1'1 which will enable the D outputs:



As described in the datasheet, you can edit the "Contents" property to specify the contents of each memory location. For example, to fill the first 4 locations of a 4-bit-wide ROM to the binary values 0000, 0101, 1010, and 1111, you could enter the following into the Contents property:

```
// comments are allowed, don't count as content lines
// 1 line per ROM location, starting at address 0
0b0000 // binary value
5      // decimal value
0xA    // hexadecimal value
0b1_11 // binary value, _ is ignored (useful for formatting)
```

Use the Jade instance below to enter your design. To complete this design problem, select the /fsm/fsm module and click  in the Jade toolbar and the built-in tester will either report any discrepancies between the expected and actual outputs, or, if your design is correct, it will record the test passed.

The tests verify that all the state transitions are correct by checking the values of U and V while the circuit is processing a sequence of IN values. You can select the "Test" tab for the /fsm/fsm to see the input sequence and the expected values of U and V at each clock cycle. The IN is changed before the rising edge of the clock and the values of U and V are checked just after the rising clock edge (i.e., after the most-recent value of IN has been processed). There are comments on each test line indicating what the state of the FSM should be after processing the new IN value.

To enable the online system to check this answer, first run the design tests provided by the tool. Open Jade in a new window