



< Previous



Next >


## WE4.1

🔖 Bookmark this page

Video explanation of solution is provided below the problem.

Truth Tables

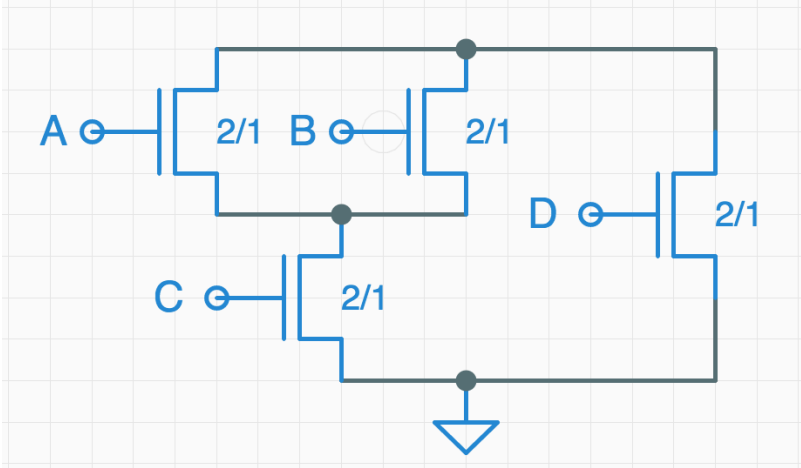16/16 points (ungraded)  
Given the CMOS circuit with pulldown shown here, and assuming that the pullup is drawn correctly, fill in the truth table for this circuit.



<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	1 ✓ Answer: 1
0	0	0	1	0 ✓ Answer: 0
0	0	1	0	1 ✓ Answer: 1
0	0	1	1	0 ✓ Answer: 0
0	1	0	0	1 ✓ Answer: 1
0	1	0	1	0 ✓ Answer: 0
0	1	1	0	0 ✓ Answer: 0
0	1	1	1	0 ✓ Answer: 0
1	0	0	0	1 ✓ Answer: 1
1	0	0	1	0 ✓ Answer: 0
1	0	1	0	0 ✓ Answer: 0
1	0	1	1	0 ✓ Answer: 0
1	1	0	0	1 ✓ Answer: 1
1	1	0	1	0 ✓ Answer: 0
1	1	1	0	0 ✓ Answer: 0
1	1	1	1	0 ✓ Answer: 0

Explanation  
From the pulldown circuit, we can generate the corresponding function that the CMOS circuit represents. The pulldown tells us that  $\overline{F} = (A + B)C + D$ . So  $F = \overline{((A + B)C + D)}$ .

Calculator

We can then plug in the given input values to determine the value of F for each combination. When A=0 B=0 C=0 and D=0, then  $(A+B)C = 0$  that ORed with  $D = 0$ , and finally the entire thing is negated, so  $F = 1$ . For A=0 B=0 C=0 and D=1,  $(A+B)C = 0 + D=1$  gives us 1 and the whole thing negated is  $F=0$ . In the same way, we can complete the rest of the truth table, and we get 1 0 1 0 0 0 1 0 0 0 1 0 0 0 for the remaining entries.

Submit

**i** Answers are displayed within the problem

Truth Tables

1/1 point (ungraded)

Can the function F defined by the following truth table be implemented as a single CMOS gate?

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Can F be implemented as a single CMOS gate?

☐ NO

☒ YES



Submit

✓ Correct (1/1 point)

Truth Tables

# CMOS Circuit to Truth Table

Calculator



# Connect

[Idea Hub](#)

[Contact Us](#)

[Help Center](#)

[Security](#)

[Media Kit](#)



© 2024 edX LLC. All rights reserved.  
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)