

<u>Help</u>





<u>Course</u> <u>Progress</u> <u>Dates</u> <u>Discussion</u> <u>Course Notes</u>

☆ Course / 4. Combinational Logic / Lecture Videos (47:49)

()

✓ Previous
✓ ■ ✓ ■ ✓ ■ ✓ ✓ ■ ✓ ✓ Next >

LE4.2

 \square Bookmark this page

■ Calculator

LE4.2.1: AND of many inputs

3/3 points (ungraded)

Suppose we wanted to build a circuit to compute the AND of 1024 separate inputs. There's good news and bad news. The bad news is that we only have 2-input AND gates (called AND2) to use when implementing the circuit. The good news is that we have as many AND2 devices as we need.

The AND2 device has a contamination delay t_{CD} of 1 ns and a propagation delay t_{PD} of 4 ns.

What is the minimum number of AND2 devices needed to implement the circuit?

Minimum number of AND2 devices needed: 1023 ✓ Answer: 1023

Considering all possible implementations, what is the smallest achievable t_{CD} ?

Smallest achievable t_{CD} (in ns): 1 \checkmark Answer: 1

Considering all possible implementations, what is the smallest achievable t_{PD} ?

Smallest achievable t_{PD} (in ns): 40 \checkmark Answer: 40

Explanation

Both the chain and tree implemenations require 1023 AND2 devices -- think about the number of "•" operators in a product term with 1024 elements.

A chain has the smallest achievable t_{CD} of 1 gate delay: consider the path from the input connected to the final gate in the chain to the output.

A tree has the smallest achievable t_{PD} of 10 gate delays since log_2 (1024) = 10. Each of the ten AND2 devices along the path from inputs to output has a t_{PD} of 4 ns.

Submit **1** Answers are displayed within the problem Discussion **Hide Discussion** Topic: 4. Combinational Logic / LE4.2 Add a Post by recent activity > Show all posts Contamination Delay? 6 How is contamination delay calculated? I must have missed this during the videos. Contamination Delay Calculation regarding shortest path? 6 Hello, In the lecture when considering the development in circuits with the help of boolean expressions we are thinking of logical bi... Previous Next >

© All Rights Reserved



⊞ Calculator

edX

About

Affiliates

edX for Business

Open edX

<u>Careers</u>

<u>News</u>

Legal

Terms of Service & Honor Code

Privacy Policy

Accessibility Policy

Trademark Policy

<u>Sitemap</u>

Cookie Policy

Your Privacy Choices

Connect

<u>Idea Hub</u>

Contact Us

Help Center

<u>Security</u>

Media Kit

















© 2024 edX LLC. All rights reserved.

深圳市恒宇博科技有限公司 <u>粤ICP备17044299号-2</u>