


For the following problems, please use the following conventions when entering boolean expressions.

- \bar{X} : enter as not(X).
- X AND Y: enter as XY.
- X AND \bar{Y} : enter as Xnot(Y).
- X OR Y: enter as X + Y.
- $\bar{X}\bar{Y}$: enter as not(X)not(Y).
- Recall that $\overline{XY} = \bar{X} + \bar{Y}$ (not $\bar{X}\bar{Y}$).
- Extra white spaces are ignored.
- Lower or upper case letters are treated the same.
- Sum of products expression refers to an expression of the form $ABC + \text{not}(A)\text{not}(B)C$, where each term is a product term and ORing them together makes a sum of products expression. Note that within a product term negation can only be applied to a single variable at a time. In other words not(A)not(B) is acceptable but not(AB) is not.

Minimal Sum Of Products

0/1 point (ungraded)

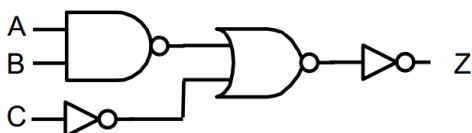Consider the following circuit that implements the 3-input function $Z(A,B,C)$:



What is the minimal sum-of-products expression for $Z(A,B,C)$:

not(b) + not(a)b + bc

✗ Answer: not(A) + not(B) + not(C)

Explanation

A simple way to solve this problem is to create Z's 8-row truth table from the circuit diagram above and see how many of the rows have a 1 at the output. We generate the following table:

A	B	C	$Z(A, B, C)$
0	0	0	1

0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

We can see that the output is 1 unless all inputs are 1. In other words, any time there is a 0 at one of the inputs, the output is 1. So, whenever A, B, or C are 0, then Z is 1. The resulting function would then be $Z = \overline{A} + \overline{B} + \overline{C}$.

Another way to think of this problem is to notice from this table that Z describes a 3 input NAND gate which in sum-of-products notation (after applying De Morgan's Law to $Z = \overline{ABC}$) is $Z = \overline{A} + \overline{B} + \overline{C}$.

Submit

 Answers are displayed within the problem

Minimal Sum Of Products

1/1 point (ungraded)

A sum-of-products expression involving 3 variables with greater than 7 product terms can *always* be simplified to a sum-of-products expression using fewer product terms.

☒ True

☐ False




Submit

✓ Correct (1/1 point)

Minimal Sum Of Products

10/10 points (ungraded)

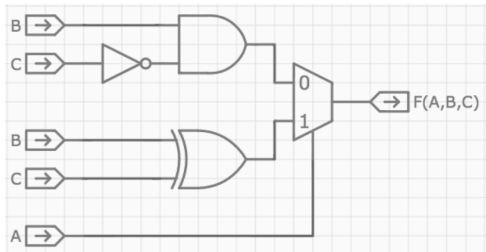A 6.004 intern at Intel has designed the combinational circuit shown below. His boss can't figure out what it does and has asked for your help.



A) Your first task is to fill out $F(A,B,C)$ in the truth table below:

A	B	C	$F(A, B, C)$
0	0	0	<input type="text" value="0"/> ✓ Answer: 0
0	0	1	<input type="text" value="0"/> ✓ Answer: 0
0	1	0	<input type="text" value="1"/> ✓ Answer: 1
0	1	1	<input type="text" value="0"/> ✓ Answer: 0
1	0	0	<input type="text" value="0"/> ✓ Answer: 0
1	0	1	<input type="text" value="1"/> ✓ Answer: 1
1	1	0	<input type="text" value="1"/> ✓ Answer: 1
1	1	1	<input type="text" value="0"/> ✓ Answer: 0

Explanation

To answer this problem, one needs to evaluate what the output of each gate will be given the particular set of inputs. In this circuit, there is a **MUX** which determines whether the top part of the circuit (**inverter** and **AND** gate) controls the output or the bottom part (**XOR**) controls it.

When $A=0$, the output is the result of the **inverter** and **AND** gate.

$A=0, B=0, C=0$: The output of the inverter is 1. The **AND** gate receives a 0 and 1 as inputs and outputs a 0. So $F(0,0,0) = 0$.

$A=0, B=0, C=1$: The output of the inverter is 0. The output of the **AND** gate is 0. So $F(0,0,1) = 0$.

$A=0, B=1, C=0$: The output of the inverter is 1. The output of the **AND** gate is 1. So $F(0,1,0) = 1$.

$A=0, B=1, C=1$: The output of the inverter is 0. The output of the **AND** gate is 0. So $F(0,1,1) = 0$.

When $A=1$, the output is the result of the **XOR** gate.

$A=1, B=0, C=0$: The output of the **XOR** is 0. So $F(1,0,0) = 0$.

$A=1, B=0, C=1$: The output of the **XOR** is 1. So $F(1,0,1) = 1$.

$A=1, B=1, C=0$: The output of the **XOR** is 1. So $F(1,1,0) = 1$.

$A=1, B=1, C=1$: The output of the **XOR** is 0. So $F(1,1,1) = 0$.

B) Now, express $F(A,B,C)$ in minimal sum-of-products form. Hint: use a Karnaugh map!

$\text{bnot}(c) + \text{anot}(b)c$

✓ Answer: $\text{Anot}(B)C + \text{Bnot}(C)$

Explanation

As the hint suggests, we can solve this problem with a Karnaugh Map. Placing the rows representing the values of A and the columns for B and C (remember to have the difference between neighboring cells be 1 bit only) we get the Karnaugh Map shown below. Looking at the cells that contain 1's, we see that we can make two groups with a size that is a power of 2. The $ABC=101$ cell has a single 1 so that will give us $\overline{A}BC$ and the rightmost column of the Karnaugh Map has two 1's so that will give us $B\overline{C}$ (A doesn't matter) giving us a final result of $F(A, B, C) = \overline{A}BC + B\overline{C}$ for the minimal sum-of-products.

		BC			
		00	01	11	10
A	0	0	0	0	1
	1	0	1	0	1

C) The boss isn't quite sure what it means but he knows his engineers are always impressed if he asks "is the circuit universal?" Is it? Choose YES or NO.

☒ YES

☐ NO


Explanation


To figure out whether a given logic circuit is universal we can check whether we can reduce it to one of the known universal sets (NAND, NOR, Inverter-And-Or). In this case we can actually use F to make a NAND since $F(1, 1, C) = \overline{C}$ and $F(A, 0, C) = AC$ - feeding the output of the latter gate through the C input of the former will give us a NAND. Since we can build a NAND out of F , it is universal since NAND is universal.

i Answers are displayed within the problem

Minimal Sum Of Products

1/1 point (ungraded)

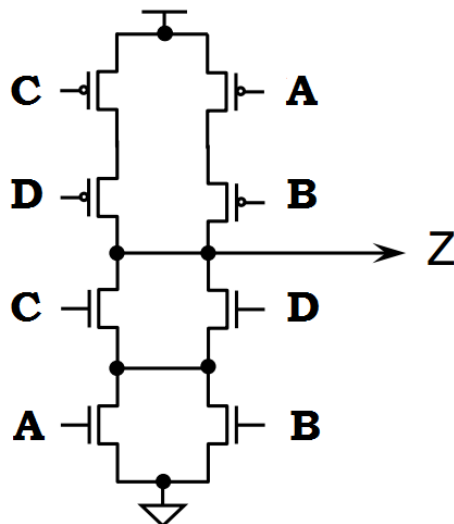Hapless Logic, Inc has found a bunch of CMOS circuits one of which is shown below:



Hapless Logic has forgotten what function, $H(A,B,C,D)$, this circuit computes so they need your help. Give a Boolean sum-of-products expression for $H(A,B,C,D)$ consistent with the pulldown shown above.

✓ Answer: $\text{not}(C)\text{not}(D) + \text{not}(A)\text{not}(B)$

Explanation

There are a number of ways of solving this problem. Remember that the pulldown circuit must be the complement of the pullup circuit and that CMOS always computes inverting logic. Looking at the pullup we can tell that when either the left branch of the path from power to Z is connected or the right branch of the path from power to Z is connected we will get a 1 at the output. The left path is on when C and D are both low (remember the pullup has PFETS). The right side is on when A and B are both low. Therefore

$$H(A, B, C, D) = \bar{C}\bar{D} + \bar{A}\bar{B}.$$

Submit

i Answers are displayed within the problem

Discussion

Hide Discussion

Topic: 4. Combinational Logic / Tutorial : Minimal Sum Of Products

Add a Post

Show all posts ▼

by recent activity ▼

- | | | |
|---|--|---|
| ? | <u>Can't understand q2 → c</u>
In the lecture i understand that any sum of product i can represent it using NAND NAND & NOR NO... | 2 |
| ✓ | <u>Universal gate ?</u>
In Question 2 my gate ends up as XOR if A=logical 1 ...is XOR universal gate ? | 3 |