



[< Previous](#)

[Next >](#)

LE8.1

Bookmark this page

Calculator

LE8.1.1 Asymptotic Latency and Throughput

1/1 point (ungraded)

If we account for fan in limitations but ignore wire delays, what is the asymptotic latency of the fastest combinational N-input AND circuit we can build?

Asymptotic latency of N-input AND:

log(N)

✓ Answer: log(N)

You entered:

$\log(N)$

Explanation

Accounting for the fan in limitations means that if we have a gate with N inputs, we can't just assume that its propagation delay is the same as a 2-input gate. The way we model this is by turning an N-input gate into a tree of 2-input gates. The equivalent tree of 2-input AND gates would have $\log(N)$ levels in the tree in order to arrive at enough 2-input AND gates to allow for N inputs. Each level of the tree must complete its propagation delay before the next level can begin its computation, therefore the latency of the tree is $\log(N)$.

Submit

❗ Answers are displayed within the problem

LE8.1.2 Asymptotic Latency and Throughput

1/1 point (ungraded)

Is $\Theta(\log_2 N)$ the same as $\Theta(\log_{10} N)$

☒ Yes

☐ No

☐ Only for some N



Explanation

According to the base-change formula for logarithms, $\text{Log}_a(n) = \frac{\text{Log}_b(n)}{\text{Log}_b(a)}$. In other words, any base can be converted to any other base by multiplying by a constant. Since we ignore constant multiplicative factors in asymptotic notation, we can also ignore bases of logarithms.

Submit

❗ Answers are displayed within the problem

LE8.1.3 Asymptotic Latency and Throughput

2 points possible (ungraded)

A combinational multiplier is pipelined for maximum throughput. If the multiplier accepts two N-bit operands, what is the appropriate "order of" notation for its throughput and latency?

Throughput $\Theta(\dots)$:

Calculator

Latency Θ (...):

Submit

Discussion

Hide Discussion

Topic: 8. Design Tradeoffs / LE8.1

Add a Post

Show all posts

by recent activity

Accounting for the fan in limitations

"... if we have a gate with N inputs, we can't just assume that its propagation delay is the same as a 2-input gate." why not?

4

< Previous

Next >

© All Rights Reserved



edX

- About
- Affiliates
- edX for Business
- Open edX
- Careers
- News

Legal

- Terms of Service & Honor Code
- Privacy Policy
- Accessibility Policy
- Trademark Policy
- Sitemap
- Cookie Policy
- Your Privacy Choices

Connect

- Idea Hub
- Contact Us
- Help Center
- Security

Calculator

[Media Kit](#)



© 2024 edX LLC. All rights reserved.
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)