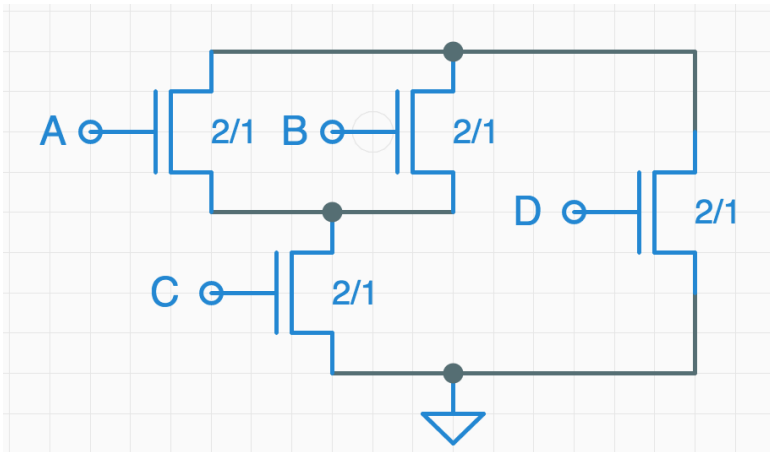


Video explanation of solution is provided below the problem.

Truth Tables

16/16 points (ungraded)

Given the CMOS circuit with pulldown shown here, and assuming that the pullup is drawn correctly, fill in the truth table for this circuit.



<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	1 ✓ Answer: 1
0	0	0	1	0 ✓ Answer: 0
0	0	1	0	1 ✓ Answer: 1
0	0	1	1	0 ✓ Answer: 0
0	1	0	0	1 ✓ Answer: 1
0	1	0	1	0 ✓ Answer: 0
0	1	1	0	0 ✓ Answer: 0
0	1	1	1	0 ✓ Answer: 0
1	0	0	0	1 ✓ Answer: 1

1	0	0	1	0	✓ Answer: 0
1	0	1	0	0	✓ Answer: 0
1	0	1	1	0	✓ Answer: 0
1	1	0	0	1	✓ Answer: 1
1	1	0	1	0	✓ Answer: 0
1	1	1	0	0	✓ Answer: 0
1	1	1	1	0	✓ Answer: 0

Explanation

From the pulldown circuit, we can generate the corresponding function that the CMOS circuit represents. The pulldown tells us that $\overline{F} = (A + B)C + D$. So

$$F = \overline{((A + B)C + D)}.$$

We can then plug in the given input values to determine the value of F for each combination. When A=0 B=0 C=0 and D=0, then (A+B)C = 0 that ORed with D = 0, and finally the entire thing is negated, so F = 1.

For A=0 B=0 C=0 and D=1, (A+B)C = 0 + D=1 gives us 1 and the whole thing negated is F=0. In the same way, we can complete the rest of the truth table, and we get 1 0 1 0 0 0 1 0 0 0 1 0 0 0 for the remaining entries.

Submit

i Answers are displayed within the problem

Truth Tables

1 point possible (ungraded)

Can the function F defined by the following truth table be implemented as a single CMOS gate?

A	B	C	F
0	0	0	1

0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Can F be implemented as a single CMOS gate?

☐ NO


☐ YES

Submit

Truth Tables

Truth Table to CMOS Circuit


A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0




▶ 0:00 / 0:00


▶ 1.0x 🔊 🗑️ 📄 🗨️

Video

 [Download video file](#)

Transcripts

 [Download SubRip \(.srt\) file](#)

 [Download Text \(.txt\) file](#)

Discussion




Hide Discussion

Topic: 4. Combinational Logic / WE4.1

Add a Post

Show all posts ▼

by recent activity ▼

- | | |
|--|---|
|  Dont't actually understand what is the definition of "a single cmos gate" | 2 |
| A circuit with only nfet as the pull-down part and pfet as the pull-up part could be defined as a sin... | |
|  F ? | 2 |
| Hi, so where is F ? | |
|  confused? | 3 |
| Hi, In the second question, why $\sim A \sim B + \sim A B + A \sim B$ could be transform into $\sim A \sim B + A \sim B + \sim A B...$ | |