

For all Beta related questions, you should make use of the [Beta documentation](#), the [Beta Instruction Summary](#), and the [Beta Diagram](#).

Beta ISA: 1

4/4 points (ungraded)

In this problem, you will consider a number of plausible hardware faults in an otherwise working Beta processor. Each of the faults involves changing a particular output of the control logic to some new (incorrect) constant value. In each case, you are to evaluate the impact of the fault on each of the following Beta instructions:

```
I1: ST(R0, 0x100, R1)
I2: JMP(LP, R31)
I3: BEQ(R31, -4, R0)
I4: SUB(R1, R0, R0)
```

For each of the following faults, identify which (if any) of the above instructions will fail to work properly – that is, if the fault might effect the processor state (register and PC values) after the execution of the instruction. Be careful: some of these are tricky!

1. ALUFN stuck at code for "-" (32-bit SUBTRACT)

Which instruction(s) fail? Select all that apply.

☒ I1

☐ I2

☐ I3

☐ I4

☐ None

2. RA2SEL stuck at 1

Which instruction(s) fail? Select all that apply.

☐ I1

☐ I2

☐ I3

☐ I4

☒ None

3. WERF stuck at 0

Which instruction(s) fail? Select all that apply.

☐ I1

☐ I2

☒ I3

☒ I4

☐ None

4. BSEL stuck at code 0

Which instruction(s) fail? Select all that apply.

☒ I1

☐ I2

☐ I3

☐ I4

☐ None

Submit

Beta ISA: 2

40/40 points (ungraded)

Marketing has asked for the following instructions to be added to an Extended Beta instruction set, for implementation on a Beta as implemented in Lecture and in the lab.

```
CLEAR2(Rx, Ry)    // Clear two registers
  Reg[Rx] ← 0
  Reg[Ry] ← 0
  PC ← PC + 4

NOR(Rx, Ry, Rz)   // Bitwise NOR: Rz[i] = NOR(Rx[i], Ry[i])
  Reg[Rz] ← bitwise NOR of Reg[Rx], Reg[Ry]
  PC ← PC + 4

LDRADR(C, Rx)     // Load Relative Address
  Reg[Rx] ← PC+4+4*SEXT(C)
  PC ← PC + 4

LDINCR(Rx, C, Ry) // Load Incremented
  EA ← Reg[Rx]+SEXT(C)
  Reg[Ry] ← Mem[EA] + 1
```

The Marketing people don't care about details of instruction coding (e.g., which fields are used to encode Rx and Ry in the above descriptions), but want to know which if any of the above can be implemented as a **single instruction** in the **existing Beta simply by changing the control ROM**.

Your job is to decide which of the above instructions can be implemented on the existing Beta, making appropriate choices for Rx and Ry, and to specify control signals that implement those instructions.

For each instruction select the appropriate values for the control signals in the table below. Select "None" for all entries in a row if the instruction cannot be implemented using the existing Beta datapath. Select "---" to indicate a "don't care" value for a control signal.

Instr	ALUFN	WERF	BSEL	WDSEL	MOE	MWR	RAZSEL	PCSEL	ASEL	WASEL
CLEAR2	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>
	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE
NOR	<div>100001</div>	<div>1</div>	<div>0</div>	<div>1</div>	<div>-</div>	<div>0</div>	<div>0</div>	<div>0</div>	<div>0</div>	<div>0</div>
	✓ Answer: 100001	✓ Answer: 1	✓ Answer: 0	✓ Answer: 1	✓ Answer: -	✓ Answer: 0	✓ Answer: 0	✓ Answer: 0	✓ Answer: 0	✓ Answer: 0
LDRADR	<div>A</div>	<div>1</div>	<div>-</div>	<div>1</div>	<div>-</div>	<div>0</div>	<div>-</div>	<div>0</div>	<div>1</div>	<div>0</div>
	✓ Answer: A	✓ Answer: 1	✓ Answer: -	✓ Answer: 1	✓ Answer: -	✓ Answer: 0	✓ Answer: -	✓ Answer: 0	✓ Answer: 1	✓ Answer: 0
LDINCR	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>	<div>NONE</div>
	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE	✓ Answer: NONE

Explanation
CLEAR2: Can't be implemented because you cannot write to two registers at the same time.
NOR: Set up the boolean operators so that they execute a NOR function. This is done by setting the two most significant bits of ALUFN to 10 to specify that its a boolean operation, and then setting the remaining four bits so that they perform the NOR function which returns 1 only when both inputs are 0. Since the encoding of the bottom 4 bits of ALUFN is abcd where *a* corresponds to both inputs being 1 and *d* corresponds to both inputs being 0, then setting abcd to 0001 results in a NOR function being implemented. So the 6 bit ALUFN is 100001. The remaining control signals follow the pattern of all other basic ALU operations (e.g., AND).
LDRADR: Making ASEL=1 provides PC+4*SEXT(C). BSEL is a don't care because the ALUFN just uses the A input. WDSEL=1 takes the ALU output as the input to the register file. This means that MOE can be a don't care. WERF=1 allows us to write to the register file. PCSEL=0 makes PC=PC+4.
LDINCR: Can't be implemented because the ALU is already in use to compute the memory read address and therefore cannot be used for the increment by 1 operation.

Submit

Answers are displayed within the problem

Beta ISA: 3

1 point possible (ungraded)
You modify a working BETA by connecting the JT input to the PCSEL MUX to the constant 0, rather than to its proper logic. Which instructions, if any, are effected by this change?

Instruction(s) effected (select all that apply):

☐ BNE

☐ JMP

☐ ADD

☐ ST

☐ None

Submit

Beta ISA: 4

3 points possible (ungraded)
For the Beta instruction sequence shown below, indicate the values of the specified quantities after the sequence has been executed.

```
. =0
CMOVE(0x6000, SP)
PUSH(SP)
HALT()
```

Value left in SP (HEX): 0x

Value pushed onto stack (HEX): 0x

Value of WDSEL control signal during CMOVE execution: 0x:

Submit

Beta ISA: 5

11 points possible (ungraded)
Many problems, like sorting, require swapping data in two memory locations. The following assembly code swaps the contents of two words in memory, with addresses stored in R0 and R1:

```
LD(R0, 0, R2)
LD(R1, 0, R3)
ST(R2, 0, R1)
ST(R3, 0, R0)
```

1. Suppose we add a SWAP instruction to the Beta. SWAP swaps the contents of a register and a memory location:

`SWAP(Ra, literal, Rc)` // Swap register contents with memory

```
EA ← Reg[Ra] + SEXT(Literal)
tmp ← Mem[EA]
Mem[EA] ← Reg[Rc]
Reg[Rc] ← tmp
PC ← PC + 4
```

Which of the following pieces of code is a valid rewrite of the code above?

☐

```
LD(R1, 0, R2)
SWAP(R1, 0, R2)
ST(R2, 0, R0)
```

☐

```
LD(R0, 0, R2)
SWAP(R1, 0, R2)
ST(R2, 0, R0)
```

☐

```
LD(R0, 0, R2)
SWAP(R1, 0, R2)
ST(R2, 0, R1)
```

☐

```
SWAP(R0, 0, R1)
```

2. Can we implement the SWAP instruction using the unpipelined Beta datapath, by simply changing the control ROM? Recall that, in the unpipelined datapath, the data memory has combinational reads, and writes are clocked, happening at the end of the cycle. Also assume that the memory still returns valid data when $WR=1$. Either fill in the control signals below, or select NONE for all cases if SWAP cannot be implemented.

Instr	ALUFN	WERF	BSEL	WDSEL	MOE	MWR	RA2SEL	PCSEL	ASEL	WASEL
SWAP	<div>Select an option ▾</div>	<div>Select an option ▾</div>	<div>Select an option ▾</div>	<div>Select an option ▾</div>	<div>Select an option ▾</div>	<div>Select an option ▾</div>	<div>Select an option ▾</div>	<div>Select an option ▾</div>	<div>Select an option ▾</div>	<div>Select an option ▾</div>

Submit

Beta ISA: 6

4 points possible (ungraded)
A "stuck-at" fault happens when a signal is shorted to VDD or GND and is permanently a logic 1 or logic 0. For each of the following stuck-at faults there is a list of instruction opcodes – please select the opcodes whose execution might be affected by the indicated fault.

1. RA2SEL stuck-at logic "0"

☐

ADD

☐

ADDC

☐

LD

☐

ST

☐

JMP

☐

BEQ

☐

BNE

☐

LDR

☐

lllop

2. BSEL stuck-at logic "1"

☐

ADD

☐

ADDC

☐

LD

☐

ST

☐

JMP

☐

BEQ

☐

BNE

☐

LDR

☐

lllop

3. WDSEL[1] (high-order bit of WDSEL mux select) stuck-at logic "0"

☐

ADD

<input type="checkbox"/> ADDC
<input type="checkbox"/> LD
<input type="checkbox"/> ST
<input type="checkbox"/> JMP
<input type="checkbox"/> BEQ
<input type="checkbox"/> BNE
<input type="checkbox"/> LDR
<input type="checkbox"/> Illop

4. WERF stuck-at logic "1"

<input type="checkbox"/> ADD
<input type="checkbox"/> ADDC
<input type="checkbox"/> LD
<input type="checkbox"/> ST
<input type="checkbox"/> JMP
<input type="checkbox"/> BEQ
<input type="checkbox"/> BNE
<input type="checkbox"/> LDR
<input type="checkbox"/> Illop

Submit

Beta ISA: 7

6 points possible (ungraded)

Your summer internship involves adding new instructions to the Beta processor. You're given a list of proposed new Beta instructions, each of which is to perform a given operation during the **single clock cycle** in which the instruction executes. You decide to sort the proposals into four classes:

- **Macro**: those instructions that can be implemented on a stock Beta, simply by defining an appropriate macro;
- **CTL**: those that can be implemented on a stock Beta, by defining an appropriate macro and making appropriate changes to the control ROM;
- **HW**: those instructions that require hardware changes beyond reprogramming the control ROM.
- **None**: The instruction as described can't be implemented, even with hardware changes.

For each of the following descriptions, identify which of the above categories the instruction falls into.

1. **ADD37(r)** which adds 37 to the contents of specified register r.

<input type="radio"/> Macro
<input type="radio"/> CTL
<input type="radio"/> Hardware
<input type="radio"/> None

2. **ZERO2(rx,ry)** which sets the contents of both registers rx and ry to zero.

<input type="radio"/> Macro
<input type="radio"/> CTL
<input type="radio"/> Hardware
<input type="radio"/> None

3. **GETPC(rx)** which sets the contents of register rx to the address of the following instruction.

<input type="radio"/> Macro
<input type="radio"/> CTL
<input type="radio"/> Hardware
<input type="radio"/> None

4. **GETADR(loc, rx)** which sets the contents of register rx to the address of a nearby location tagged loc.

<input type="radio"/> Macro

☐ CTL

☐ Hardware

☐ None

5. **ISMEMZERO(rx,ry)** which sets the contents of register ry to the 1 if the main memory location whose address is in register rx contains zero, else ry is set to 0.

☐ Macro

☐ CTL

☐ Hardware

☐ None

6. **BITCLEAR(rx,ry)** which clears (sets to zero) the bits of register ry for which the corresponding bits of rx have the value 1; other bits of ry are left unchanged.

☐ Macro

☐ CTL

☐ Hardware

☐ None

Submit

Beta ISA: 8

10 points possible (ungraded)
Marketing has asked for the following instruction to be added to an Extended Beta instruction set, for implementation on an unpipelined Beta.

```
BGT(Rx, Ry, C )
EA ← PC+4+4*SEXT(C)
If Reg[Rx] > Reg[Ry] then PC ← EA
else PC ← PC + 4
```

The Marketing people don't care about details of instruction coding (e.g., which fields are used to encode Rx and Ry in the above descriptions), but want to know if **BGT** can be implemented as a **single instruction** in the **existing Beta simply by changing the control ROM**. If so, fill in the appropriate values for the control signals in the table below. Otherwise, select NONE for each control signal. Use "-" to indicate a "don't care" value for a control signal.

Instr	ALUFN	WERF	BSEL	WSEL	MOE	MWR	RA2SEL	PCSEL	ASEL	WASEL
BGT	<div>Select an option</div>	<div>Select an option</div>	<div>Select an option</div>	<div>Select an option</div>	<div>Select an option</div>	<div>Select an option</div>	<div>Select an option</div>	<div>Select an option</div>	<div>Select an option</div>	<div>Select an option</div>

Submit

Discussion

Topic: 13. Building the Beta / Tutorial: Beta ISA

Hide Discussion

Add a Post

<div>Show all posts</div>	<div>by recent activity</div>
<div><div><div>Beta ISA 6 part C</div><div>"WSEL[1] (high-order bit of WSEL mux select) stuck-at logic "0": makes it impossible to set WSEL = 2 which is required for any type of load operation. So LD...</div><div>5</div></div></div>	
<div><div><div>NOR in Beta ISA : 2</div><div>I am not able to understand the explanation provided for NOR function to be implemented with ALU. I am just clueless as to what is it trying to say in the explanati...</div><div>5</div></div></div>	
<div><div><div>Tip for entering NONes en masse</div><div>(This probably doesn't work on every OS/browser, but it works in Chrome on Windows) Click the first field, then hit the END key, and keep alternating TAB and EN...</div><div>2</div></div></div>	
<div><div><div><input checked="" type="checkbox"/> TP 7.D - Beta ISA - GETADR(lox, Rx) - Why not 'macro'?</div><div>I might be misunderstanding something, but I believe this instruction: GETADR(loc, rx) can be replaced by a single macro: CMOVE(loc, rx) given that Joe is simply...</div><div>3</div></div></div>	
<div><div><div>[STAFF] MOE when using ST</div><div>Hi, Control logic table says MOE should be 0 when using ST. Why MOE should be 0 and no "Don't Care". If WSEL is "Don't Care" and WERF is 0, MOW could be...</div><div>2</div></div></div>	