



- Course
- Progress
- Dates
- Discussion
- Course Notes

🏠 Course / 4. Combinational Logic / Lecture Videos (47:49)



< Previous

Next >


LE4.6

🔖 Bookmark this page

Calculator

LE4.6.1: Mux Logic

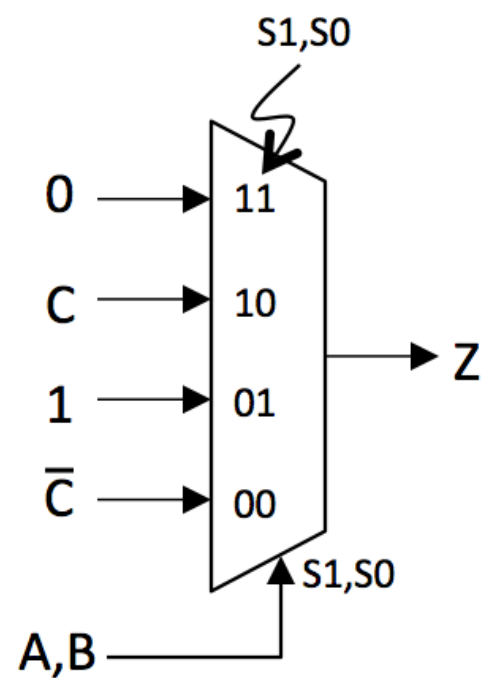8/8 points (ungraded)
Consider the following schematic for a mux-based implementation for a 3-input, 1-output Boolean function.



Please fill in the truth table below, giving the value of the output Z for the eight possible combinations of the inputs values A, B, and C.

A	B	C	Z
0	0	0	<div>1</div> <div>✓ Answer: 1</div>
0	0	1	<div>0</div> <div>✓ Answer: 0</div>
0	1	0	<div>1</div> <div>✓ Answer: 1</div>
0	1	1	<div>1</div> <div>✓ Answer: 1</div>
1	0	0	<div>0</div> <div>✓ Answer: 0</div>
1	0	1	<div>1</div> <div>✓ Answer: 1</div>
1	1	0	<div>0</div> <div>✓ Answer: 0</div>
1	1	1	<div>0</div> <div>✓ Answer: 0</div>

Explanation

The first two rows of the truth table are filled with \overline{C} .
The next two rows of the truth table are filled with 1.
The next two rows of the truth table are filled with C .
The last two rows of the truth table are filled with 0.

Submit

Answers are displayed within the problem

Discussion

Hide Discussion

Topic: 4. Combinational Logic / LE4.6

Add a Post

Show all posts

by recent activity

Can't understand the diagram or how to solve

So a Mux is a data selector given the selector inputs. The selector inputs correspond to the 4 inputs, 0, 1, C and not C. And I'm assuming th...

Calculator

☒ Can't understand diagram.

I can't understand the information conveyed by the diagram. What is the meaning of the curved arrow? I have no idea about anything regar...

2

[← Previous](#)

Next >

© All Rights Reserved



edX

[About](#)

Affiliates

edX for Business

Open edX

Careers

[News](#)

Legal

Terms of Service & Honor Code

[Privacy Policy](#)

Accessibility Policy

Trademark Policy

[Sitemap](#)

[Cookie Policy](#)

Your Privacy Choices

Connect

Idea Hub

[Contact Us](#)

[Help Center](#)

Security

Media Kit



© 2024 edX LLC. All rights reserved.

深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)

Calculator