

[Course](#)

[Progress](#)

[Dates](#)

[Discussion](#)

[Course Notes](#)

 [Course](#) / [4. Combinational Logic](#) / [Tutorial Problems](#)



< Previous





Next >

Tutorial : Combinational Timing

 Bookmark this page

Combinational Timing

1/1 point (ungraded)

Is it possible for an inverter to have a contamination delay that is greater than its propagation delay?

☐ Yes


☒ No

☐ Can't Tell



Explanation

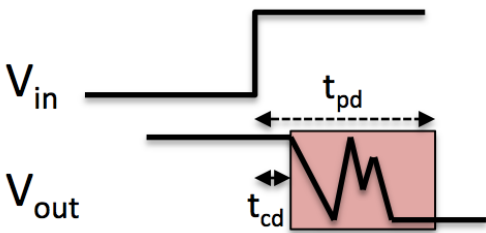By definition, the contamination delay of any gate must be less than or equal to the propagation delay of that gate. Taking a look at an inverter specifically, you can visualize this using the following diagram.




If you think of the input changing instantaneously as shown here, and just think about what happens to your output, then its clear that $t_{CD} < t_{PD}$. t_{CD} measures the time from when the input changes to when the output might begin to change. t_{PD} measures the time from when the input changes to when the output becomes stable and valid with its new value. The output must enter the red zone (t_{CD}) before it can exit it (t_{PD}).

Submit

i Answers are displayed within the problem

Combinational Timing

2 points possible (ungraded)

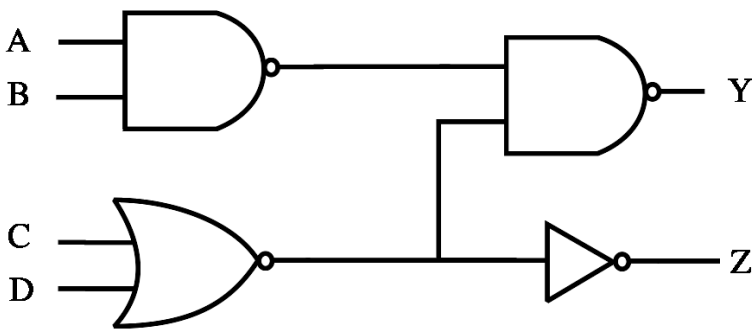

Here's a table showing the t_{CD} and t_{PD} for each of the components in the circuit above. Please compute t_{CD} and t_{PD} for the circuit as a whole.

	t_{CD}	t_{PD}
Inverter	0 ns	4 ns
NAND	1 ns	8 ns
NOR	4 ns	10 ns

Calculator


Contamination delay (ns):

Propagation delay (ns):

Submit

Combinational Timing

2 points possible (ungraded)

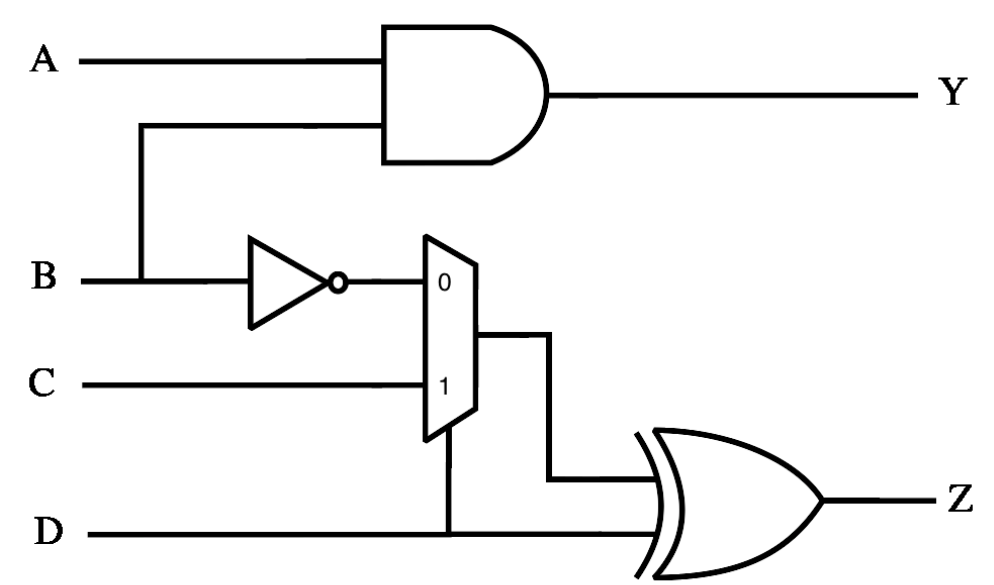

Here's a table showing the t_{CD} and t_{PD} for each of the components in the circuit above. Please compute t_{CD} and t_{PD} for the circuit as a whole.

	t_{CD}	t_{PD}
Inverter	0.1 ns	0.7 ns
AND2	0.3 ns	0.7 ns
XOR2	0.4 ns	2.2 ns
MUX2	0.1 ns	1.0 ns

t_{CD} (ns):

t_{PD} (ns):

Submit

Discussion

Hide Discussion

Topic: 4. Combinational Logic / Tutorial : Combinational Timing

Add a Post

Show all posts by recent activity

[STAFF] there is no E in 2nd graph!

Also too many paragraphs in the answer to 2nd circuit. It is a simple concept 2 paragraphs should be enough

2

Combinational Timing_Part 1

6

Calculator



edX

- [About](#)
- [Affiliates](#)
- [edX for Business](#)
- [Open edX](#)
- [Careers](#)
- [News](#)

Legal

- [Terms of Service & Honor Code](#)
- [Privacy Policy](#)
- [Accessibility Policy](#)
- [Trademark Policy](#)
- [Sitemap](#)
- [Cookie Policy](#)
- [Your Privacy Choices](#)

Connect

- [Idea Hub](#)
- [Contact Us](#)
- [Help Center](#)
- [Security](#)
- [Media Kit](#)



© 2024 edX LLC. All rights reserved.
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)