



< Previous

Next >


LE6.4

Bookmark this page

Calculator

LE6.4.1 Metastability in latches

5/6 points (ungraded)

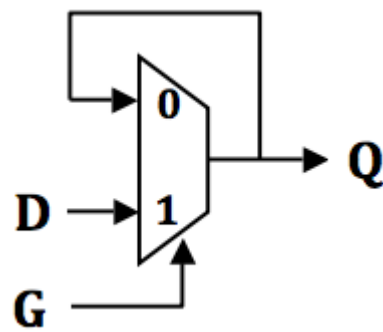

Assume that we have made a transparent latch using a lenient 2-input MUX as shown above. The lenient MUX has a propagation delay of t_{PD} and a contamination delay of t_{CD} .

A certain sequence of inputs -- violating the dynamic discipline -- has caused the Q output to assume an invalid voltage. You have observed the voltage at Q at this value for an interval many times larger than t_{PD} , despite valid stable inputs at D and G during this interval.

For each of the following statements, please indicate either TRUE or FALSE, assuming you are observing an invalid Q output after this relatively long interval of valid D and G inputs.

(A) The G input must be 0.

☐ True

☒ False

✗

Explanation

A invalid output can only persist when the latch is in "memory mode", i.e., when G is 0. When G is 1, the latch is a simple combinational device which will produce a valid and stable output within t_{PD} of a transition on the D input.

(B) The D input must be 1.

☐ True

☒ False

✓

Explanation

The metastable condition is caused by entering memory mode when Q is near the metastable voltage, which can happen on both a rising or falling transition on D.

(C) Setting and holding G=1 (while D remains valid and stable) will assure a stable value at Q after a delay of t_{PD} .

☒ True

☐ False

✓

Explanation

As mentioned in the explanation for (A), when G is 1, the latch is a simple combinational device which will produce a valid and stable output within t_{PD} of a transition on the D input.

(D) Setting and holding $G=1$ for t_{PD} and returning it to 0 for another t_{PD} (while D remains valid and stable) will assure that the value at D appears at Q.

☐ True

☒ False



Explanation
The second 1-to-0 transition on G doesn't meet the latch's setup time, which may cause the latch to go metastable again. If G had been 1 for $2 \cdot t_{PD}$ then the value at D would have been guaranteed to be the value at Q.

(E) If the inputs remain unchanged (stable and valid) for an interval of T seconds, the probability of a valid Q output at the end of this interval increases exponentially with T.

☒ True

☐ False



Explanation
The probability of a positive feedback loop being metastable decreases exponentially with time.

(F) Assuming the valid stable inputs remain at D and G, once Q leaves the metastable state and reaches a valid logic level it is guaranteed to have the same value as D.

☐ True

☒ False



Explanation
A metastable latch can resolve to either of the two possible stable states, independently of the value of D. Bascially, metastability causes the latch to "forget" the D input value.

Submit

Answers are displayed within the problem

Discussion

Hide Discussion

Topic: 6. Finite State Machines / LE6.4

Add a Post

Show all posts

by recent activity

[Increasing exponentially.](#)

3

< Previous

Next >



edX

- About
- Affiliates
- edX for Business
- Open edX
- Careers
- News

Legal

- Terms of Service & Honor Code
- Privacy Policy
- Accessibility Policy
- Trademark Policy
- Sitemap
- Cookie Policy
- Your Privacy Choices

Connect

- Idea Hub
- Contact Us
- Help Center
- Security
- Media Kit



© 2024 edX LLC. All rights reserved.
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)