



< Previous

Next >

# CMOS logic gates

Bookmark this page

Calculator

Lab due Oct 24, 2016 21:59 -02    Past due

CMOS logic gates

0.0/2.0 points (graded)

There are 16 possible 2-input combinational logic gates. The cost of implementing these gates varies dramatically, requiring somewhere between 0 and 10 mosfets depending on the gate. For example, it takes 2 mosfets to implement  $F = \overline{A}$  but 4 mosfets (organized as two inverters) to implement  $F = A$ .

For each of the 2-input gates whose Karnaugh maps are given below, indicate the minimum number of mosfets required to implement the gate. You should only consider static fully-complementary circuits like those shown in the presentations; these implementations meet the following criteria:

- no static power dissipation
- $V_{OL} = 0V$ ,  $V_{OH}$  = power supply voltage
- NFETs appear only in pulldown circuits, PFETs appear only in pullup circuits
- the pullup and pulldown are complementary, i.e., when one path is "on", the other is "off"
- the pullup and pulldown circuits can be decomposed into series and parallel connections of mosfets
- all gate implementations restore incoming logic levels (so a wire connecting an input terminal to an output terminal would not be a legal gate implementation)

		A	
$\overline{A}$	$+ B$	0	1
		0	1
B	0	1	0
	1	0	0

Number of MOSFETs need to implement NOR:

4

Answer: 4

		A	
$\overline{A}$	$\cdot B$	0	1
		0	1
B	0	0	0
	1	0	1

Number of MOSFETs need to implement AND:

6

Answer: 6

		A	
$\overline{A}$	$\oplus B$	0	1
		0	1
B	0	0	1
	1	1	0

Number of MOSFETs need to implement XOR:

12

Answer: 10

Hint: see discussion in following design problem.

		A	
$\overline{B}$		0	1
		0	1
B	0	1	1
	1	0	0

Number of MOSFETs need to implement  $\overline{B}$ :

2

Answer: 2

		A	
$\overline{A}$	$\cdot \overline{B}$	0	1
		0	1
B	0	0	1
	1	0	0

Number of MOSFETs need to implement  $A \cdot \overline{B}$ :

Answer: 6

Submit

Discussion

Topic: Assignment 2 (due Oct 24) / CMOS logic gates

Hide Discussion

Add a Post

◀ All Posts

Calculator

# XOR using 10 gates only !!

question posted 7 years ago by [atarief](#)

I solved the xor gate using 12 gates. How possible to make it work with only 10 gates ? Thanks

This post is visible to everyone.

Add a Response

1 response

**Ferdinandzanni**

7 years ago

Try this expression:  $\text{not}(\text{not}(A)+B) + \text{not}(A+\text{not}(B))$ .

Add a comment

Showing all responses

Add a response:

Preview

Submit

< Previous

Next >

© All Rights Reserved



edX

[About](#)

[Affiliates](#)

[edX for Business](#)

[Open edX](#)

[Careers](#)

[News](#)

Legal

[Terms of Service & Honor Code](#)

[Privacy Policy](#)

[Accessibility Policy](#)

[Trademark Policy](#)

Calculator

[Sitemap](#)  
[Cookie Policy](#)  
[Your Privacy Choices](#)

# Connect

[Idea Hub](#)  
[Contact Us](#)  
[Help Center](#)  
[Security](#)  
[Media Kit](#)



© 2024 edX LLC. All rights reserved.  
深圳市恒宇博科技有限公司 [粤ICP备17044299号-2](#)