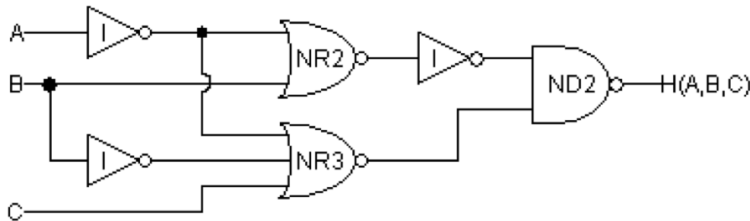


LE3.5.1: Timing

2/2 points (ungraded)

Consider the following circuit that implements the 3-input function $H(A,B,C)$:



Using the following table of timing specifications for each component, what are the contamination delay t_{CD} and the propagation delay t_{PD} for the circuit shown above?

<u>gate</u>	<u>t_{CD}</u>	<u>t_{PD}</u>
I	3ps	15ps
ND2	5ps	30ps
NR2	5ps	30ps
NR3	10ps	50ps

t_{CD} (in picoseconds):

13

✓ Answer: 13

t_{PD} (in picoseconds):

95

✓ Answer: 95

Explanation



Shortest path for t_{CD} is NR2 + I + ND2. So $t_{CD} = 5 + 3 + 5 = 13ps$.

Longest path for t_{PD} is I + NR3 + ND2. So $t_{PD} = 15 + 50 + 30 = 95ps$.

Submit

i Answers are displayed within the problem

Discussion

[Hide Discussion](#)**Topic:** 3. CMOS / LE3.5**Add a Post**Show all posts by recent activity 

? why isn't the longest path (I + NR2 +I + ND2) ? and the shortest path (NR3 + ND2)?
why isn't the longest path (I + NR2 +I + ND2) ? and the shortest path (NR3 + ND2)? please explain...

7 