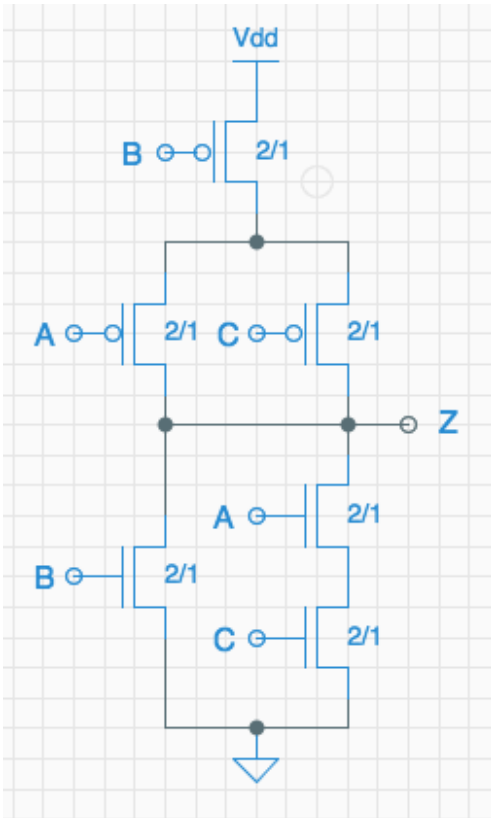


CMOS

1/1 point (ungraded)

Given the following cmos gate, determine the function computed by this gate.



☐ A) $Z = B \cdot (A + C)$

☐ B) $Z = B + A \cdot C$

☒ C) $Z = \overline{B} \cdot (\overline{A} + \overline{C})$

☐ D) $Z = \overline{B} + \overline{A} \cdot \overline{C}$

☐ E) None of the above



Explanation

Looking at the pulldown circuitry for this gate, we see that $Z = \overline{B + A \cdot C}$. To simplify this, we use DeMorgan's Law to find that $Z = \overline{B} \cdot \overline{A \cdot C} = \overline{B} \cdot (\overline{A} + \overline{C})$.

Submit

i Answers are displayed within the problem

CMOS

1/1 point (ungraded)

What is the minimum number of NFETs required to build a CMOS circuit (perhaps involving more than one CMOS gate) that has the following truth table?

<i>A</i>	<i>B</i>	<i>C</i>	<i>G</i>
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

☐ A) 3

☐ B) 4

☒ C) 5

☐ D) 6

☐ E) None of the above




Submit

✓ Correct (1/1 point)

CMOS

2/2 points (ungraded)

 Consider the following circuit that implements the 3-input function $Z(A,B,C)$:



Which of the proposals below is the best way to shorten the rise time of the signal at Z?

P1: Add two additional series-connected inverters to the output.

P2: Double the width of the NFET in the output inverter.

P3: Double the width of the PFET in the output inverter.

P4: Halve the width of the NFET in the output inverter.

P5: Halve the width of the PFET in the output inverter.

Best proposal: P3 ✓ Answer: P3

Explanation

Making the PFETs wider will make it so that when the output is switching from 0 to 1, the PFETs will conduct more and the output will be pulled up to vdd more quickly.

Can the function $Z(A, B, C)$ be implemented as a single 3-input CMOS gate having complementary pullup/pulldown circuits?

Implement as a single CMOS gate? YES ✓ Answer: YES

Explanation

The truth table for this circuit is the following:

A	B	C	$Z(A, B, C)$
0	0	0	1
0	0	1	1

0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

This is equivalent to \overline{ABC} , which is a 3-input NAND gate. We know that NAND gates can be implemented as a single CMOS gate, so the answer is YES.

Submit

i Answers are displayed within the problem

Discussion

Hide Discussion

Topic: 4. Combinational Logic / Tutorial : CMOS Continued

Add a Post

Show all posts ▼

by recent activity ▼

? Why more current causes faster rise time?

2

I'm not surprised though, but why exactly is that? I don't remember learning it in the course.